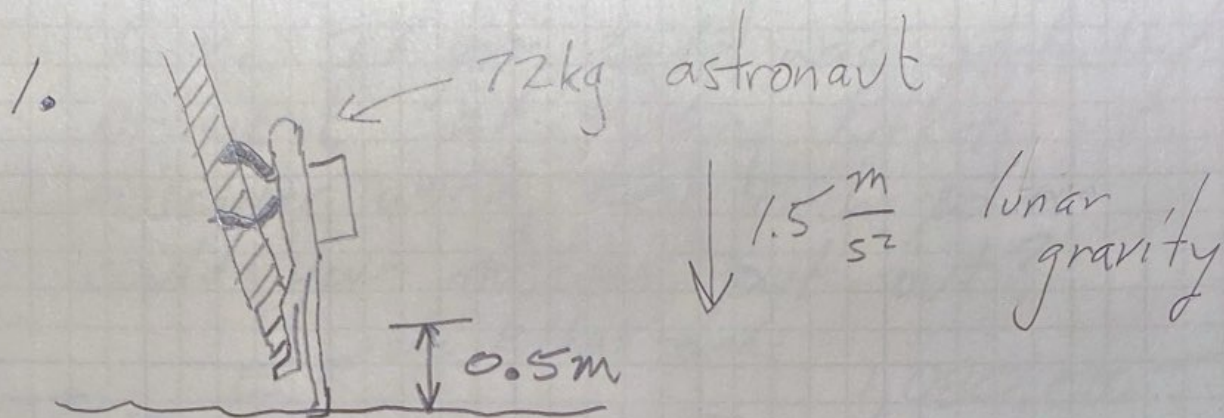


SEPT. 14

1/8

Problem Set 1 - with solutions



Energy released is $72 \text{ kg} \cdot 0.5 \text{ m} \cdot \frac{1.5 \text{ m}^2}{\text{s}^2}$

That's $48 \text{ kg} \frac{\text{m}^2}{\text{s}^2}$ $1 \text{ kg} \frac{\text{m}^2}{\text{s}^2} \equiv 1 \text{ J}$

So the energy released is 48 J.

2. A 50g "serving" of KitKat water bars has 259 kcal of energy.

the unit nutritionists use

the unit chemists used in the 1800s

That's 25,900 cal of energy

a. $1 \text{ cal} \equiv 4.184 \text{ J}$. How many Joules are in the 50g serving?

$$259,000 \text{ cal} \cdot \frac{4.184 \text{ J}}{\text{cal}} = 1,080,000 \text{ J}$$

↑
I rounded to 3 significant figures

2b. You are hiking, and you have $\frac{2}{3}$ one of those 50g "servings" every hour. If your body was perfectly efficient at turning KitKats into muscular work, how much power could your muscles put out?

$$P \equiv \frac{E \leftarrow \text{one KitKat serving}}{t \leftarrow \text{every hour}} = \frac{1,080,000 \text{ J}}{3600 \text{ s}}$$

$$= 300 \frac{\text{J}}{\text{s}}$$

$$1 \text{ W} \equiv \frac{1 \text{ J}}{1 \text{ s}}$$

$$= 300 \text{ W}$$

3a. 5 Coulombs of charge "falls" through an electrical potential and releases 150 J of energy. What is the electrical potential?

$$V \equiv \frac{E}{Q} = \frac{150 \text{ J}}{5 \text{ C}} = 30 \frac{\text{J}}{\text{C}}$$

$$1 \frac{\text{J}}{\text{C}} \equiv 1 \text{ V}$$

$$V = 30 \text{ V}$$

I started using script V for voltage (aka electrical potential) so that it is distinguished from Roman V for Volts.

$$3b. \quad 20A \text{ is } 20 \frac{C}{s}$$

3/8

20C "falling" through 12V is 240J.
That is happening every second. So the
power is $P = \frac{E}{t} = \frac{240J}{s} = 240W$

4a. A proton has charge of $1.6 \times 10^{-19} C$.
I'm splitting the question into two parts.
How many protons make 1C?

$$\frac{1C}{1.6 \times 10^{-19} \frac{C}{\text{proton}}} = \frac{1}{1.6} \times 10^{19} \text{ protons}$$

$$= 0.625 \times 10^{19} \text{ protons}$$

$$= 6.25 \times 10^{18} \text{ protons}$$


$$\frac{1}{1.6} = \frac{1}{8/5} = \frac{5}{8}$$

$$= 0.625$$

4b. If the LHC at CERN carries
0.58A in its beam, how many protons
pass by the particle detectors in 1 second?

$$0.58A \times 1s = 0.58C$$

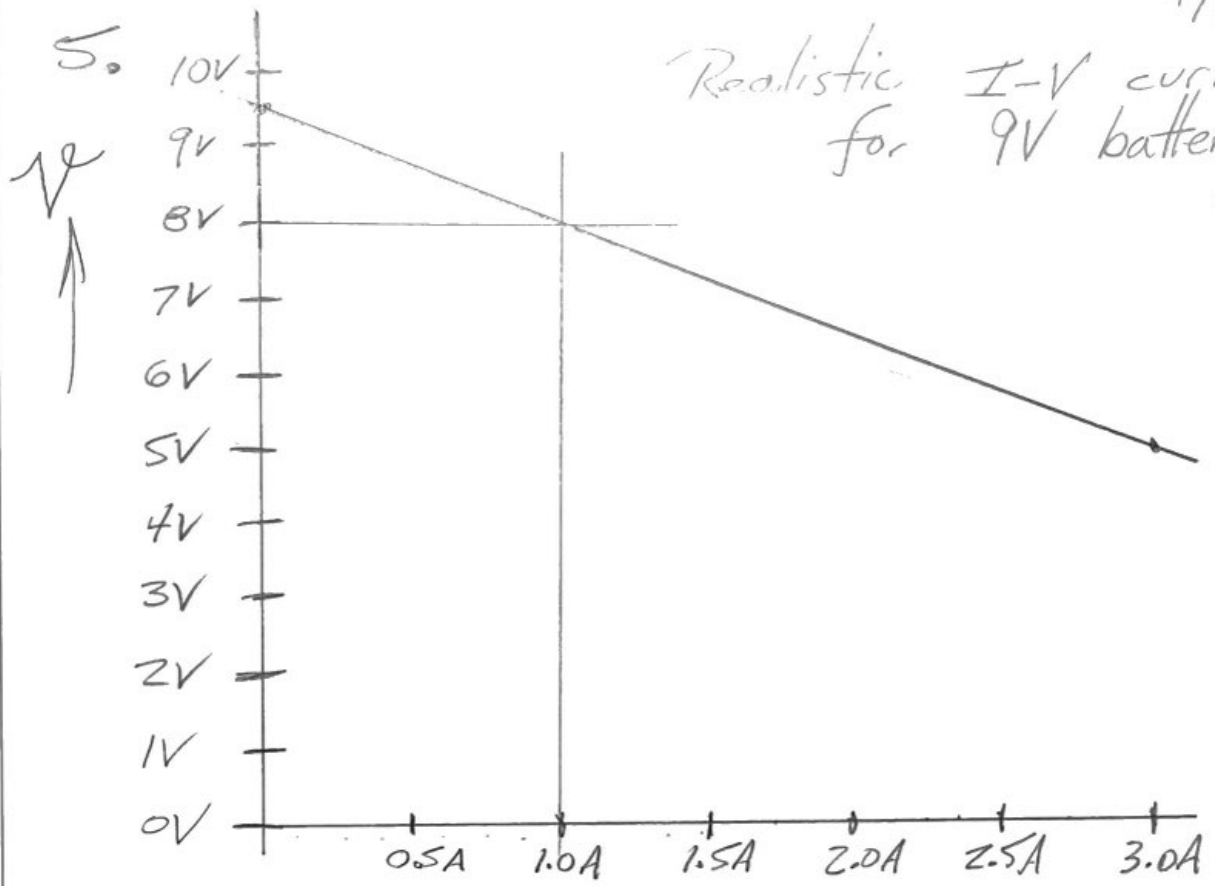
$$0.58C \times 6.25 \times 10^{18} \frac{\text{protons}}{C} = 3.6 \times 10^{18} \text{ protons}$$



The more current that is drawn from the battery, the less voltage it delivers.

A realistic battery can be modeled as a perfect voltage source and a resistor.

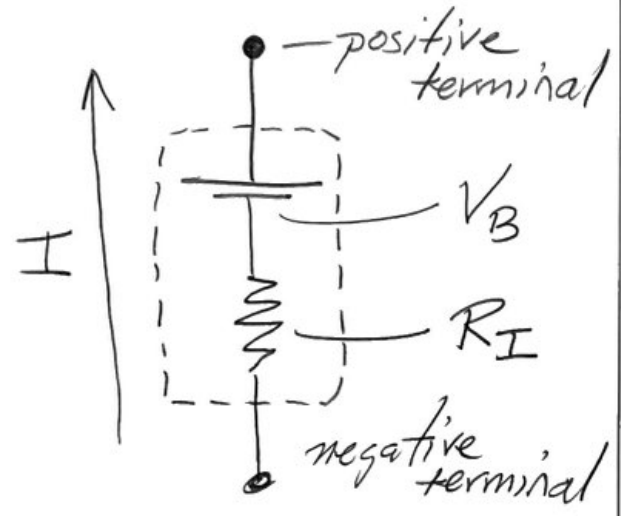What is in the dotted lines models the realistic battery



5/8


5a. From the graph, determine V_B .
When no current is flowing we read 9.5V off the graph. So $V_B = 9.5V$

5b. From the graph, determine R_I .
When 1A is flowing, the battery's voltage has dropped to 8V. That is a drop of 1.5V relative to when no current is flowing.

The resistor must be responsible for that 1.5V drop in voltage.

$$R_I = \frac{1.5V}{1A} = 1.5 \Omega$$

6a. (This was mis-numbered as 5a.)

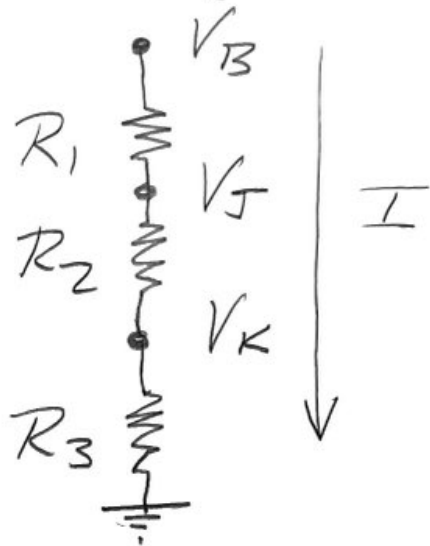

Determine V_J and V_K in terms of V_B , R_1 , R_2 , and R_3 . I is also an unknown that shouldn't appear in your answers.

6a. (CONT'D) Voltage across R_1 is $V_B - V_J$
 " " R_2 is $V_J - V_K$
 " " R_3 is $V_K - 0$
 Ohm's Law applied to each resistor:

$$IR_1 = V_B - V_J$$

$$IR_2 = V_J - V_K \quad (*)$$

$$IR_3 = V_K - 0 \quad (**)$$

Quick way to find I so you can eliminate it: add all three equations.

$$IR_1 + IR_2 + IR_3 = V_B - V_J + V_J - V_K + V_K - 0$$

$$I(R_1 + R_2 + R_3) = V_B$$

$$I = \frac{V_B}{R_1 + R_2 + R_3}$$

Now use the $(**)$ equation to find V_K .

$$V_K = IR_3 = V_B \frac{R_3}{R_1 + R_2 + R_3}$$

Then use the $(*)$ equation to find V_J .
I skipped a couple of steps

$$V_J = V_K + IR_2 = V_B \frac{R_2 + R_3}{R_1 + R_2 + R_3}$$

6b. (This was mis-numbered as 5b.) ^{7/8}


Plug in $V_B = 10V$ $R_1 = 800\Omega$
and $R_2 = R_3 = 100\Omega$

$$V_J = 10V \frac{100\Omega + 100\Omega}{800\Omega + 100\Omega + 100\Omega}$$
$$= 10V \frac{200\Omega}{1000\Omega} = 10V \cdot \frac{2}{10} = 2V$$

$$V_K = 10V \frac{100\Omega}{1000\Omega} = 10V \cdot \frac{1}{10} = 1V$$

Can you see why this is called a voltage divider?

7a. (This was mis-numbered as 6a.)

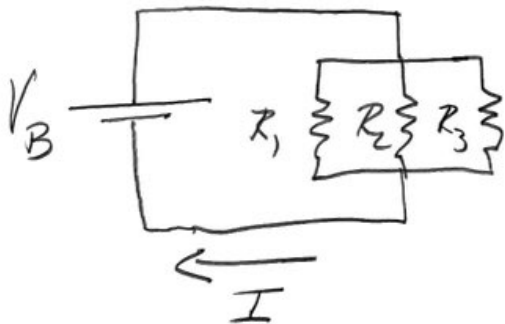

Find I in this circuit.

Each resistor has a voltage V_B applied to it. Therefore

$$I_1 = \frac{V_B}{R_1} \quad I_2 = \frac{V_B}{R_2} \quad I_3 = \frac{V_B}{R_3}$$

7a. (CONT'D) The total current ^{8/8}

$$I = I_1 + I_2 + I_3 = \frac{V_B}{R_1} + \frac{V_B}{R_2} + \frac{V_B}{R_3}$$
$$= V_B \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

7b. Rearrange the equation to solve for $\frac{V_B}{I}$

$$\frac{V_B}{I} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

This shows that the three resistors in parallel act as if they are a single resistor whose resistance is:

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

This is more commonly written as:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$